 


Running Time of Carry- Lookahead Adder


Running time of CLA

$N = 16$ bits

$k = 4$ bits



(a)

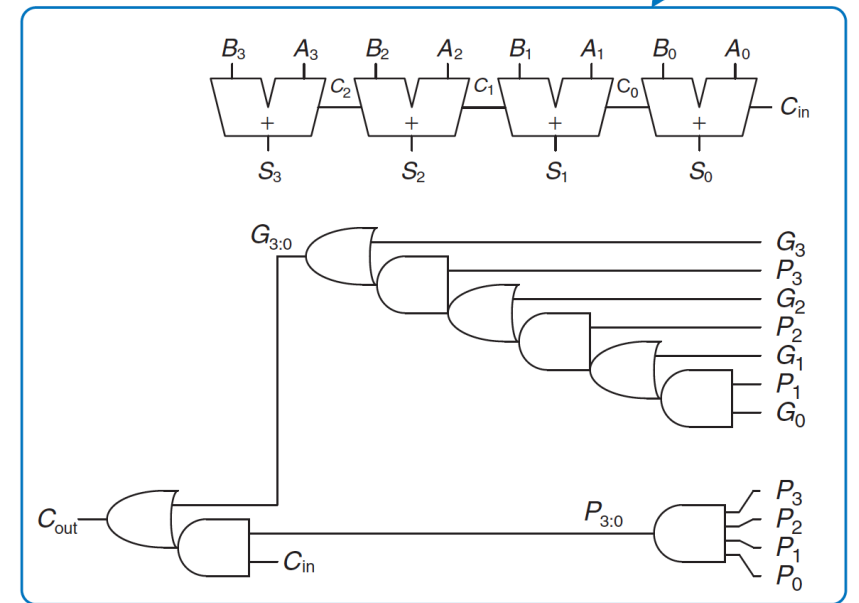

(b)

$$t_{CLA} = t_{pg} + t_{pg_block} + \left(\frac{N}{k} - 1 \right) t_{AND_OR} + k t_{FA}$$

Running time of CLA

$$t_{CLA} = t_{pg} + t_{pg_block} + \left(\frac{N}{k} - 1\right)t_{AND_OR} + kt_{FA}$$

Not as easy to compare apples-to-apples against CSA because not entirely written in terms of T_{FA}

Completely possible to do, but requires more work than it's worth for this course

Instead, consider cost asymptotically and how it varies with block size

Running time of CLA

$$t_{CLA} = t_{pg} + t_{pg_block} + \left(\frac{N}{k} - 1\right)t_{AND_OR} + kt_{FA}$$

Same tradeoff as before:

Large k means we have more adders on critical path

Small k means carry needs to go through more blocks

Use the same trick and set $k = \sqrt{N}$ – overall time once again grows as $O(\sqrt{n})$

For your project, CSA will generally be slightly faster

Running time of CLA vs Ripple-Carry

Compare delay of Ripple Carry and CLA.

Assume:

Full Adder Delay: 300ps

2 input gate delay: 100ps

$N = 16$ bits

$k = 4$ bits

$$t_{\text{ripple}} = Nt_{FA}$$

$$t_{CLA} = t_{pg} + t_{pg_block} + \left(\frac{N}{k} - 1\right)t_{AND_OR} + kt_{FA}$$

Even faster adders

Idea of carry-lookahead can be repeated in hierarchical way to improve asymptotic time to $O(\log(n))$

Your book calls these prefix adders, though some sources simply refer to them as carry-lookahead adders

We will not cover these in lecture, but they aren't *that* bad, and it is not uncommon for a few groups to implement one in JLS