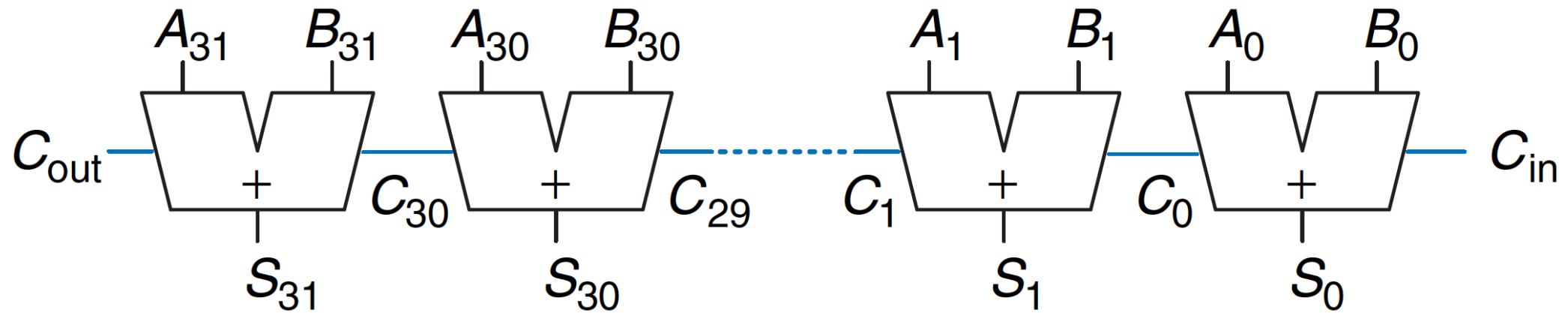


Carry-Lookahead Adder

Ripple Carry Adder



Carry-Lookahead Adder

Waiting for propagation of carry is expensive all the way through
adder is expensive

Saw with carry-select adders that we can do work in parallel to
decrease total time at cost of additional hardware

Carry-select adders duplicate everything (twice as many full adders as
ripple-carry adder)

In reality, computing the carry is the slowdown, so we can save some
hardware by focusing on precomputing just the carry

Carry-Lookahead Adder


Use same general trick as carry-select – do most of the work in parallel, before carry-in arrives

Big picture:


- Divide adder into blocks

- Include separate circuitry to calculate the carry out from each block

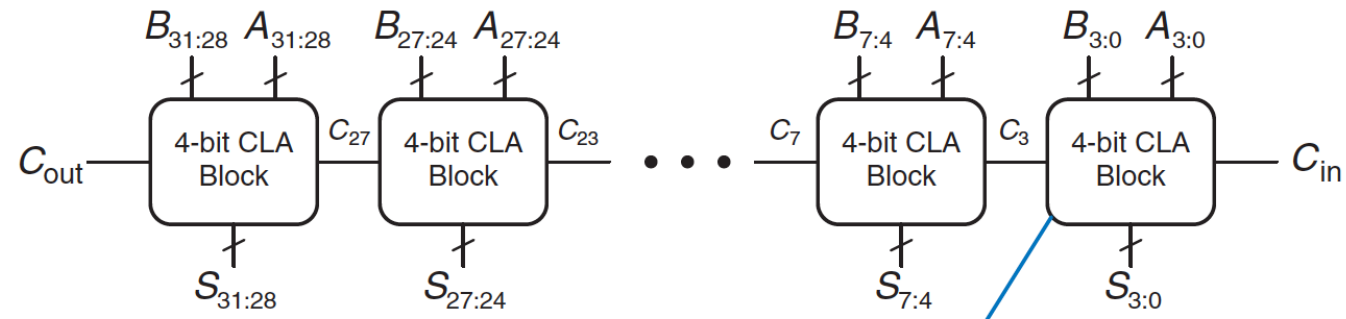- Most of work for carry-out is precomputed in all blocks at once



(a)

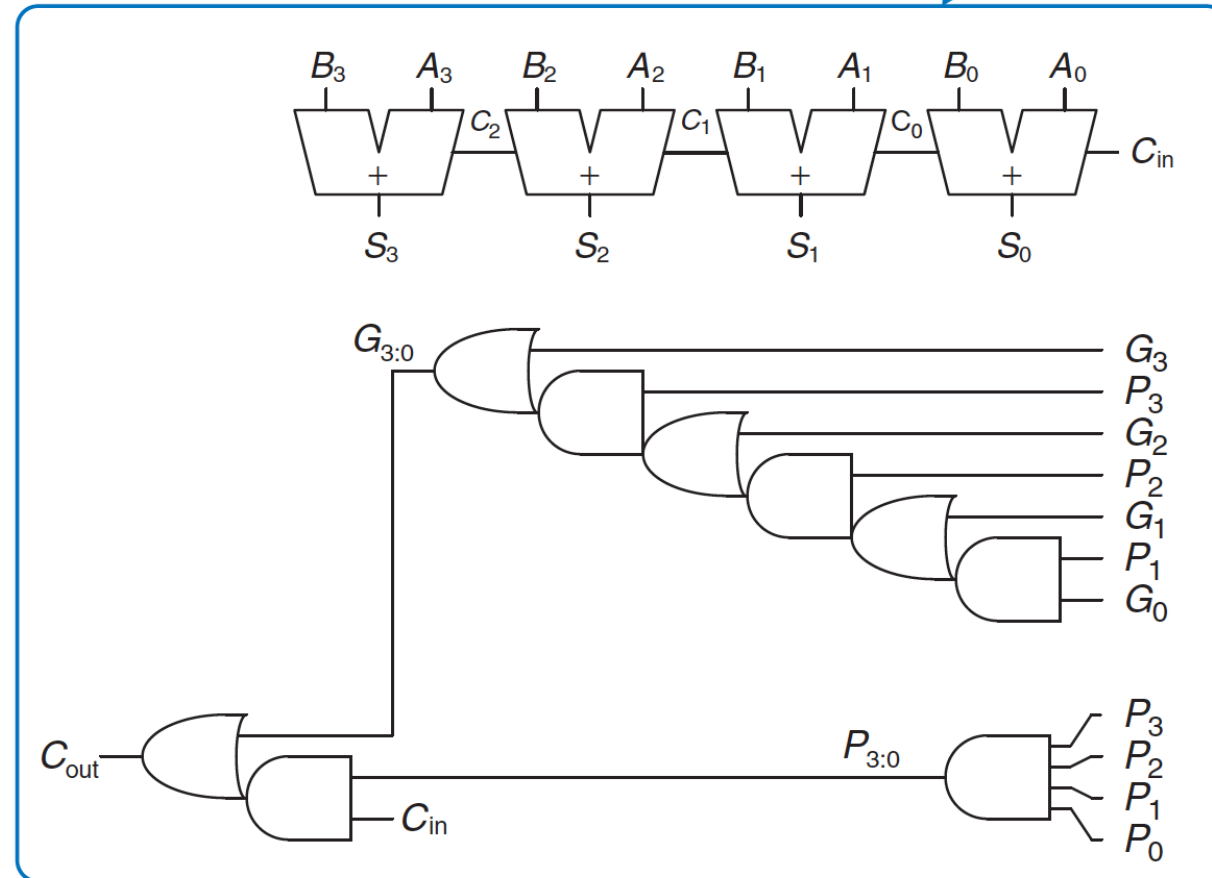

(b)

Computing Carry-out

Simple enough to determine whether single column of sum results in carry-out

Pay attention to “generate” vs “propagate” terminology

$$\begin{array}{r} 0101_2 \\ + 0111_2 \\ \hline \end{array}$$

Computing Carry-out

i_{th} column *generates* carry if it produces carry out independent of carry in

A and B are 1

$$G_i = A_i B_i$$

i_{th} column *propagates* carry if there is carry out whenever there is carry in

A or B are 1

$$P_i = A_i + B_i$$

Computing Carry-out

For individual column of sum:

$$C_i = A_i B_i + (A_i + B_i) C_{i-1} = G_i + P_i C_{i-1}$$

$$\begin{array}{r} 0101\ 0100\ 1001_2 \\ +\ 0111\ 1101\ 0110_2 \\ \hline \end{array}$$

Extends to Blocks


Block *generates* carry if it produces a carry out independent of carry in

Block *propagates* carry if it produces a carry out when there is a carry in


$$G_{3:0} = G_3 + P_3(G_2 + P_2(G_1 + P_1G_0))$$

$$P_{3:0} = P_3P_2P_1P_0$$

$$C_i = G_{i:j} + P_{i:j}C_j$$

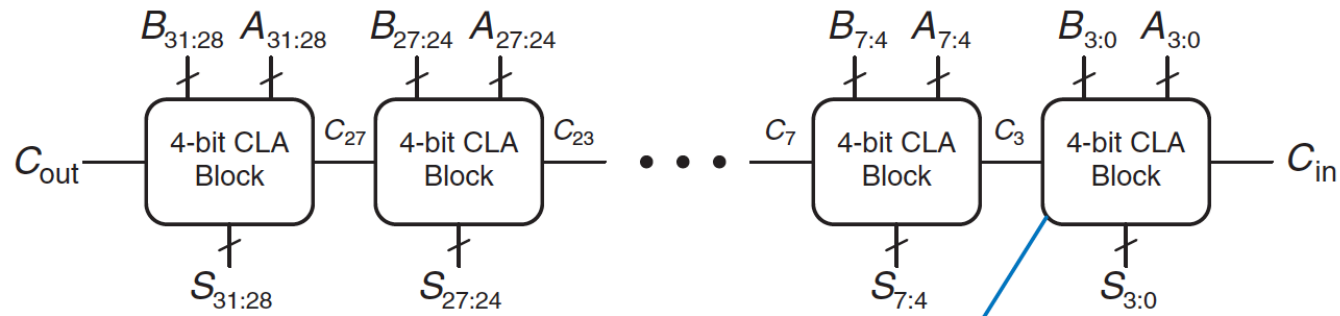

(a)


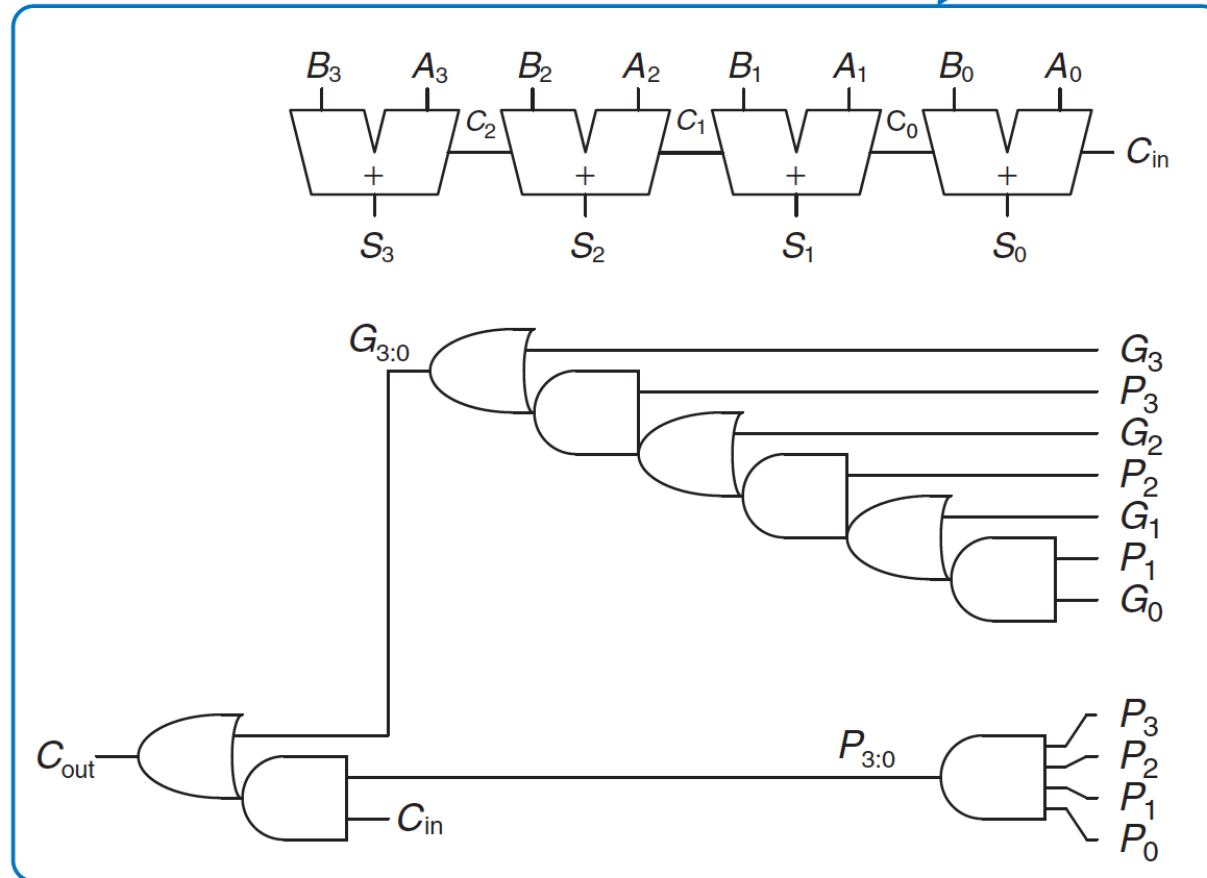


(b)


$$G_{3:0} = G_3 + P_3(G_2 + P_2(G_1 + P_1G_0))$$

$$P_{3:0} = P_3P_2P_1P_0$$



$$C_i = G_{i:j} + P_{i:j}C_j$$

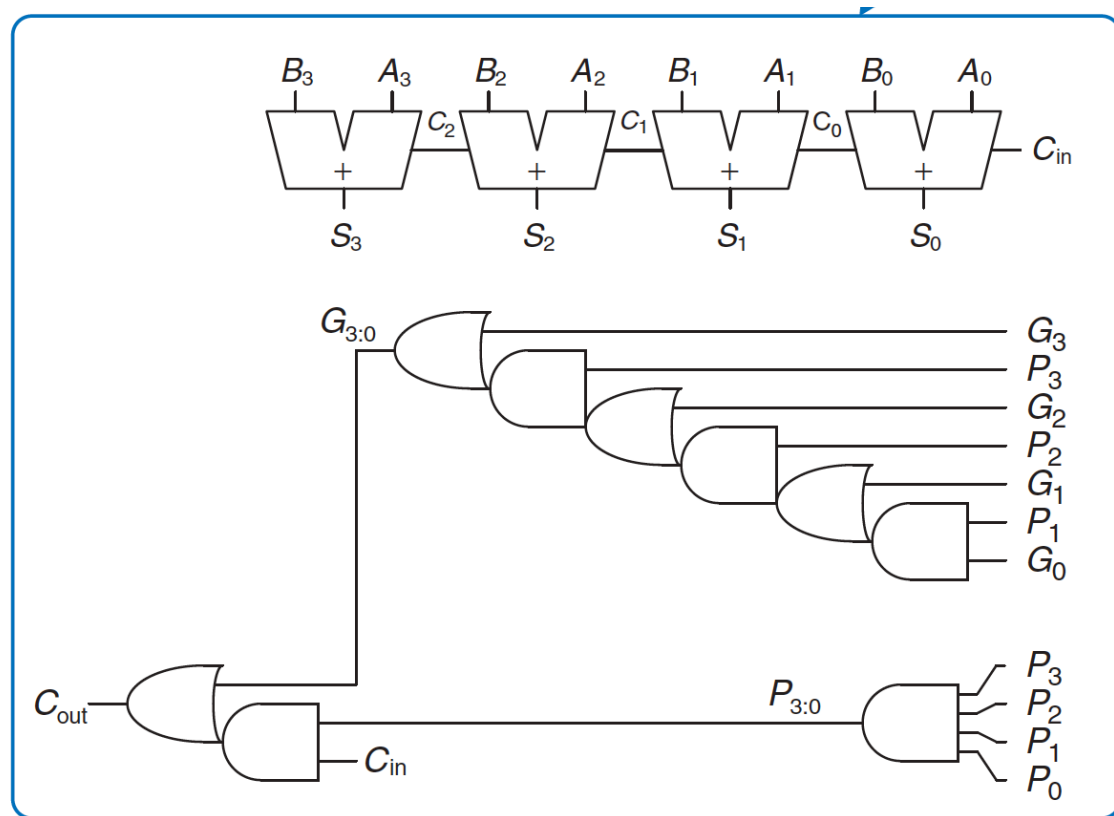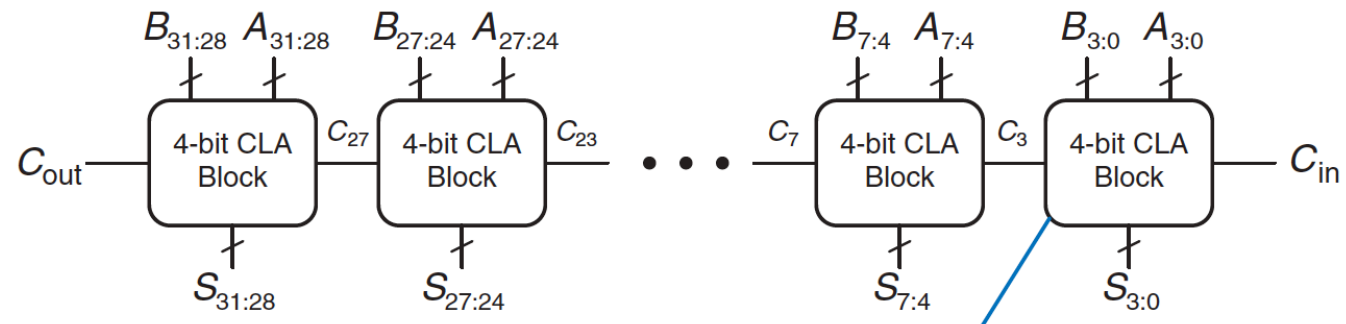


(b)

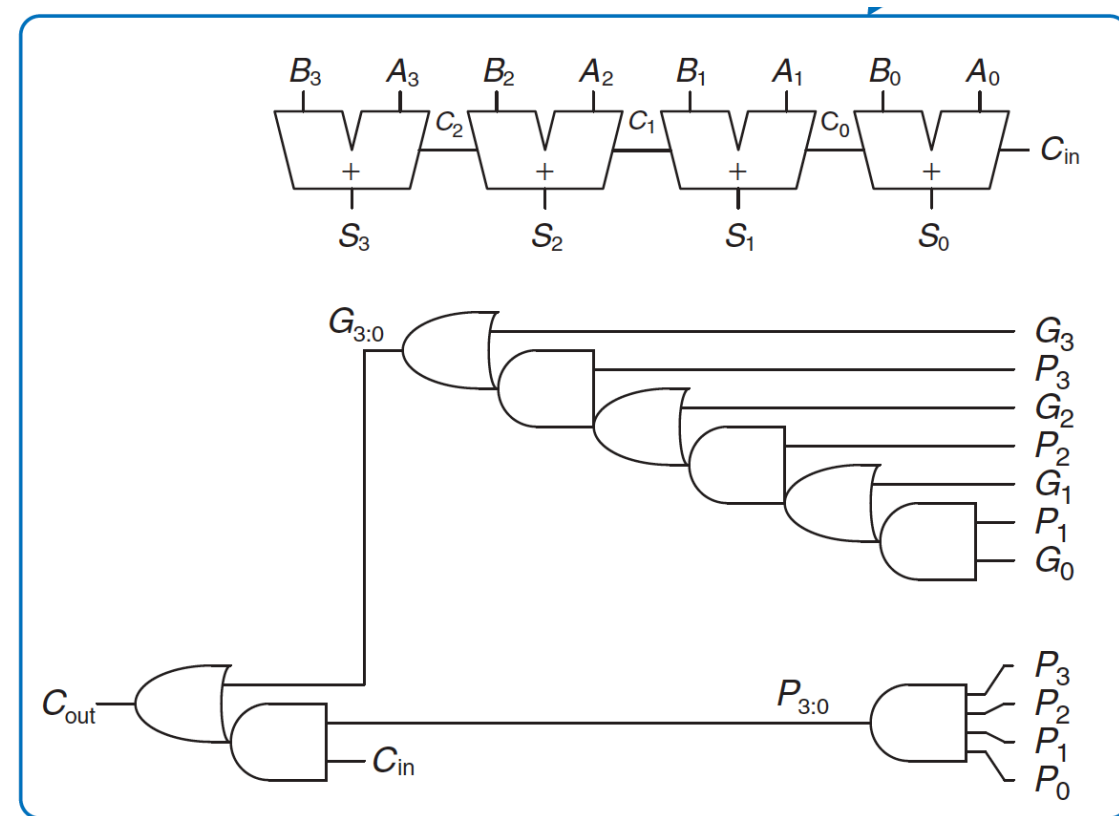


(b)

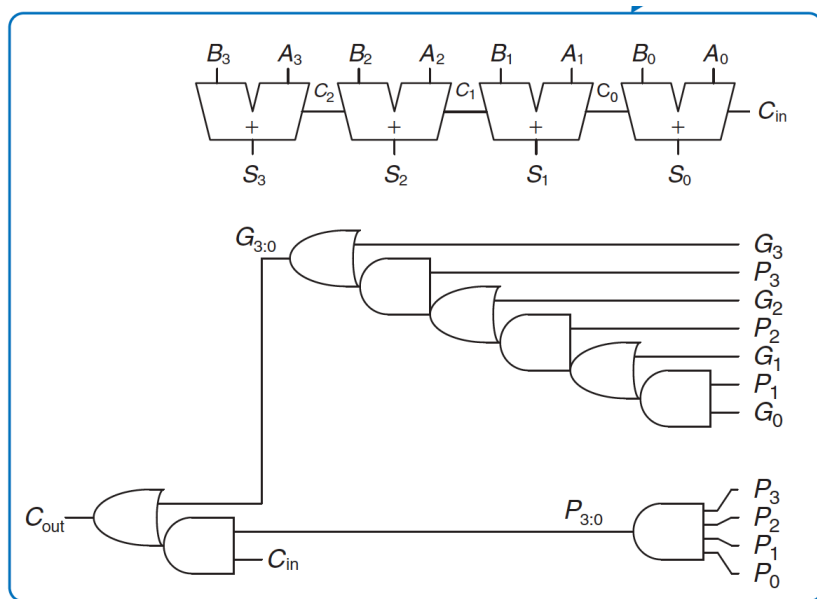 

(b)

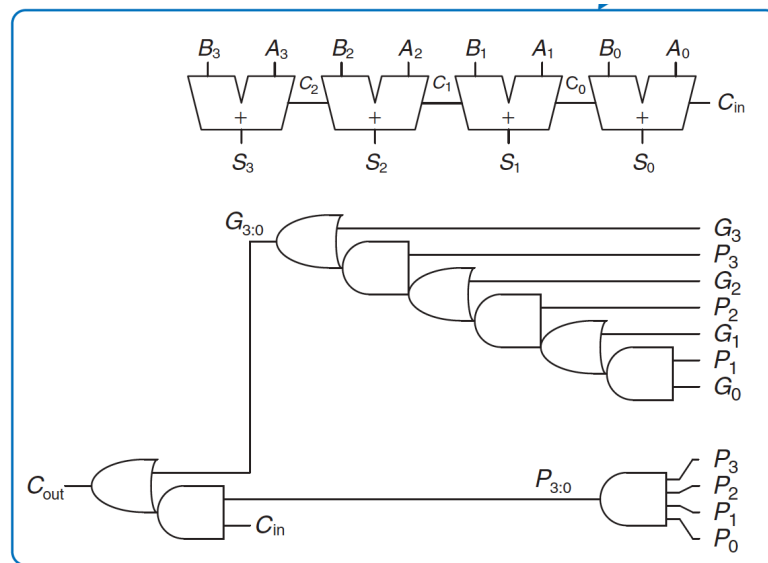

(b)

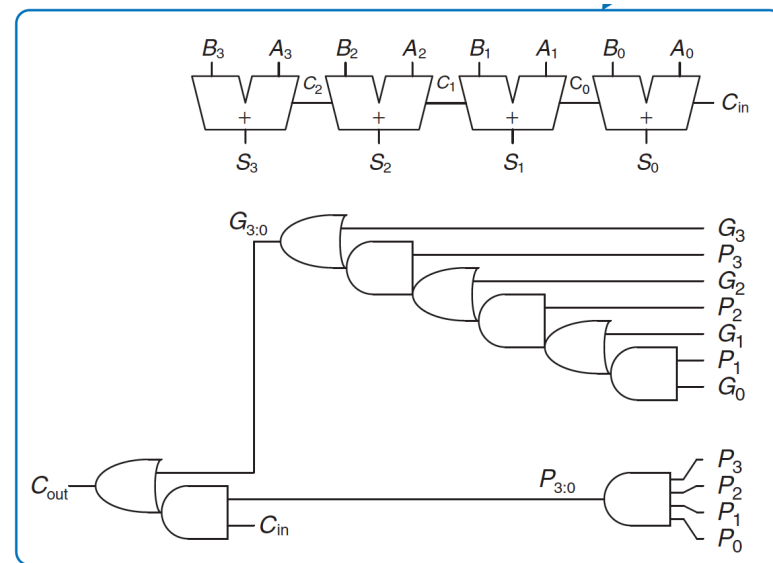

(b)

Steps to CLA

- Step 1:
 - First block starts computing S_0 through S_3 using ripple-carry adder
 - **All blocks** compute $G_{i:j}$ and $P_{i:j}$
- Step 2:
 - First block finishes computing C_3 using just two gates and precomputed $G_{3:0}$ and $P_{3:0}$
- Step 3:
 - Second block receives C_3
 - Second block computes C_7 using just two gates and precomputed $G_{7:4}$ and $P_{7:4}$
 - Second block starts computing S_4 through S_7 using ripple-carry adder
 - While S_4 through S_7 are being computed, C_3 is already passed to next block
 - ... and so on