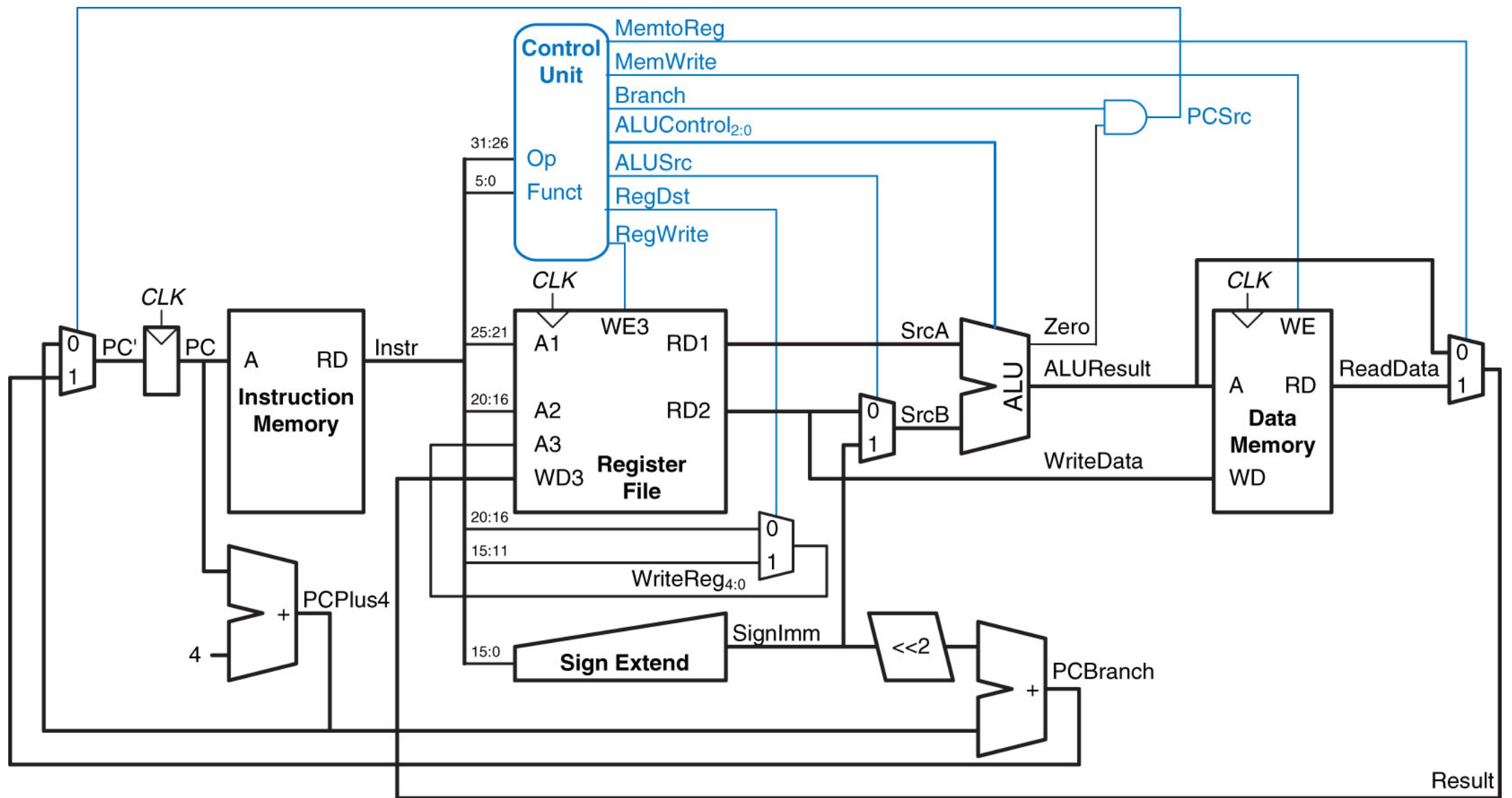


# MIPS Control Logic



# Handling various instruction types

Our single circuit acts as one of several different circuits depending on instruction

When add instruction read, does one thing, but when beq instruction read, does a different thing

Muxes allow one circuit to handle all of the different MIPS instructions

Control logic tells the muxes how to behave

# Implementing control logic

How can control logic know what to do for particular instruction?


Simple – because you know what each mux should do for particular instruction

Designer essentially creates lookup table for each mux for each instruction

For example, when circuit sees opcode for add, sets `ALUSrc` to 0

# Control Inputs

Instruction	Opcode	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

 

# Boolean algebra

Of course, by now we are too good at designing circuits to want to use a simple lookup table

How big would the table need to be to determine, e.g., ALUOp for every single opcode and function code combination?

# Boolean algebra

Of course, by now we are too good at designing circuits to want to use a simple lookup table

How big would the table need to be to determine, e.g., ALUOp for every single opcode and function code combination?

6-bit opcode, 6-bit function code

$2^{12} = 4096$ . We can do much better by looking for patterns



# Control Inputs

First, recall something about our R-type circuits – every instruction used same datapath!


Only ALUOp needs to change among various R-type instructions

Instruction	Opcode	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

# Control Inputs

Perhaps using the same opcode for all R-type instructions was not such a strange idea after all!

Instruction	Opcode	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

 

# Control Inputs

We can create smaller circuits to determine value of each control wire

Instruction	Opcode	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01


# Control Inputs

We can create smaller circuits to determine value of each control wire

Assuming CPU supported only instructions listed below, how would you create circuit that takes opcode as input and outputs RegWrite?

Instruction	Opcode	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

# RegWrite

 


Instruction	Opcode	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemtoReg	ALUOp
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

# ALU decoder

ALU decoder is its own small circuit (as we saw previously)

Design in the same way – it's all combinational circuits at this point

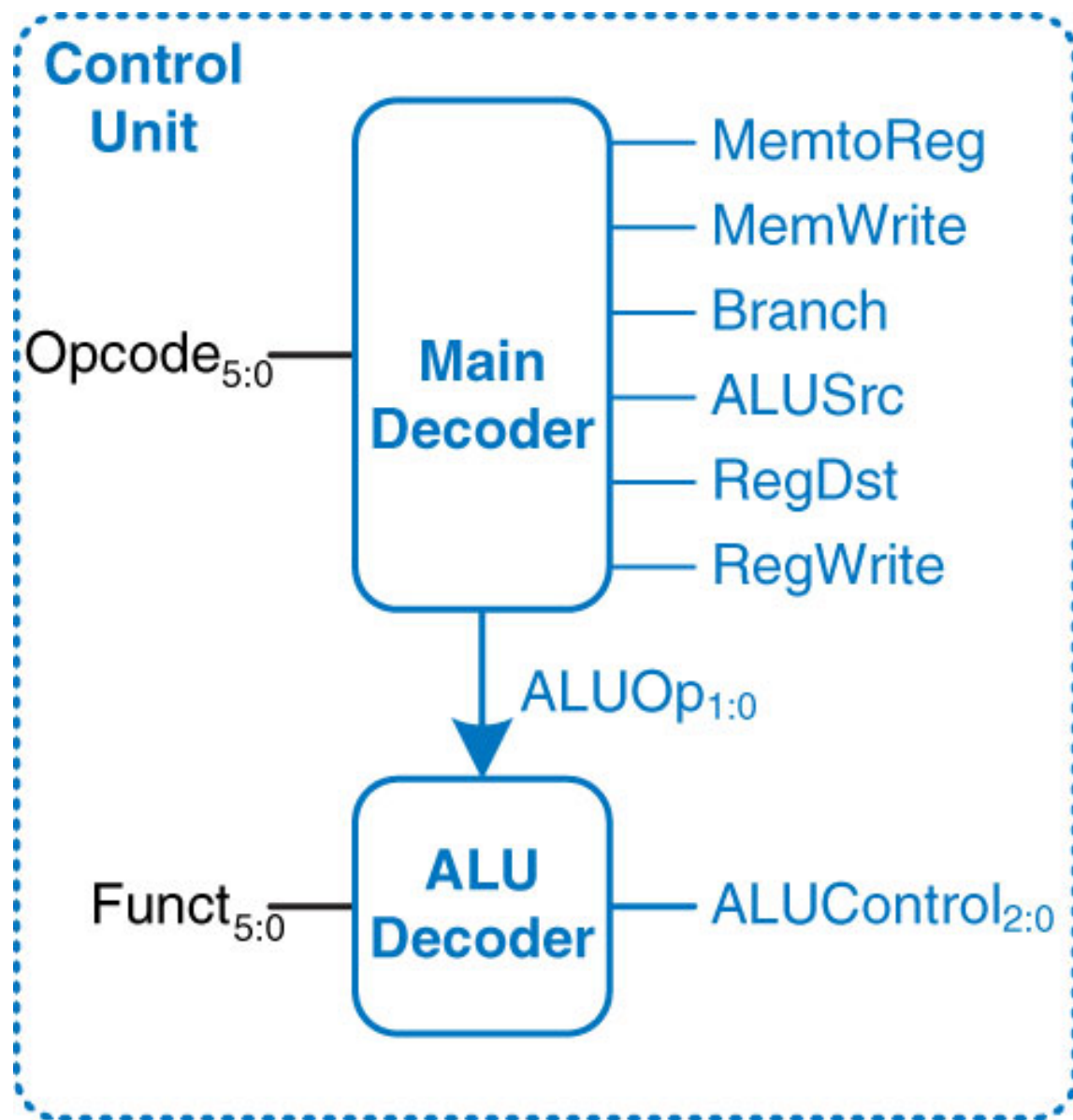Has 3-bit output instead of 1-bit, but you've designed circuits with more than one bit of output before





# ALU Decoder

ALUOp	Meaning
00	add
01	subtract
10	look at funct field
11	n/a

ALUOp	Funct	ALUControl
00	X	010 (add)
X1	X	110 (subtract)
1X	100000 (add)	010 (add)
1X	100010 (sub)	110 (subtract)
1X	100100 (and)	000 (and)
1X	100101 (or)	001 (or)
1X	101010 (slt)	111 (set less than)

# Control logic

Two keys to figuring out control logic:

1. You have to know what you want the circuit to do
2. Once you use that information to make a table, you can use all your usual tricks to turn that into a combinational circuit

# OR instruction? (R-type)

