

Boolean Algebra

Adapted from slides by Jared Moore

Boolean Algebra

Equations that we have previously discussed are not necessarily the most efficient!

$$Y = AB + AC$$

Key: Not always a straightforward process to simplify.

Axioms

- Rules that are assumed to be correct.
- Unprovable as they are definitions.
- Use them to prove all theorems of Boolean Algebra

Duality: If symbols 0 and 1 and the operators AND and OR are interchanged, the statement will still be correct.

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Working in binary.

NOT Behavior



Axiom

Dual

Name

A1 $B = 0$ if $B \neq 1$

A1' $B = 1$ if $B \neq 0$

Binary field

A2 $\bar{0} = 1$

A2' $\bar{1} = 0$

NOT

A3 $0 \bullet 0 = 0$

A3' $1 + 1 = 1$

AND/OR

A4 $1 \bullet 1 = 1$

A4' $0 + 0 = 0$

AND/OR

A5 $0 \bullet 1 = 1 \bullet 0 = 0$

A5' $1 + 0 = 0 + 1 = 1$

AND/OR

AND Behavior



OR Behavior




Theorems


Use to simplify equations and circuits

Key: Remove Gates!

	Theorem		Dual	Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

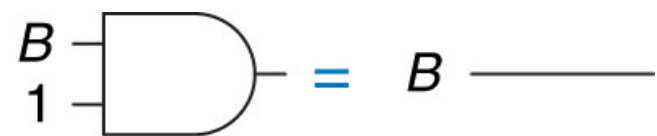


(a)

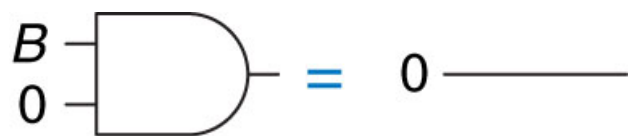


(a)




(a)

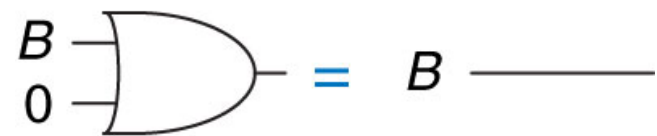


(b)

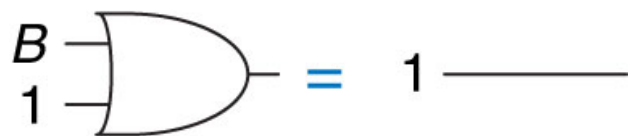


(b)

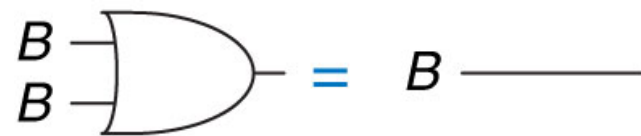

(b)

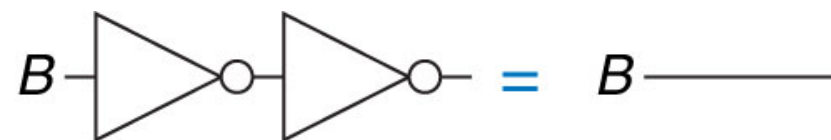

(a)

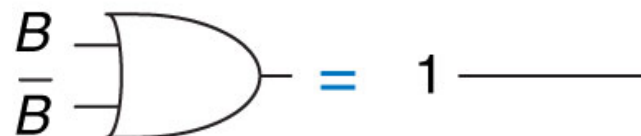

(b)

	Theorem		Dual	Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + (B \bullet D) = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots)$	De Morgan's Theorem

Some are not similar to algebra

For example, in standard algebra, addition does not distribute over multiplication.

$$\text{T8} \quad (B \bullet C) + (B \bullet D) = B \bullet (C + D) \quad \text{T8'} \quad (B + C) \bullet (B + D) = B + (C \bullet D) \quad \text{Distributivity}$$

Eliminate Redundant Variables

T9 – T11 allow us to eliminate redundant variables.
(We'll give this a try later in examples.)

$$\text{T9} \quad B \bullet (B + C) = B$$

$$\text{T9'} \quad B + (B \bullet C) = B$$

Covering

$$\text{T10} \quad (B \bullet C) + (B \bullet \overline{C}) = B$$

$$\text{T10'} \quad (B + C) \bullet (B + \overline{C}) = B$$

Combining

$$\begin{aligned} \text{T11} \quad & (B \bullet C) + (\overline{B} \bullet D) + (C \bullet D) \\ & = B \bullet C + \overline{B} \bullet D \end{aligned}$$

$$\begin{aligned} \text{T11'} \quad & (B + C) \bullet (\overline{B} + D) \bullet (C + D) \\ & = (B + C) \bullet (\overline{B} + D) \end{aligned}$$



Consensus

De Morgan's Theorem

The complement of the product of all the terms is equal to the sum of the complement of each term.

Powerful tool for circuit design



NAND

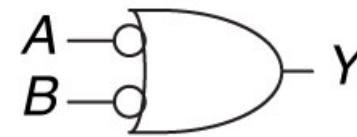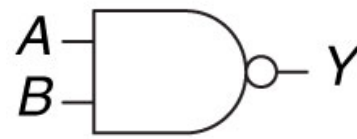

$$Y = \overline{AB} = \bar{A} + \bar{B}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR

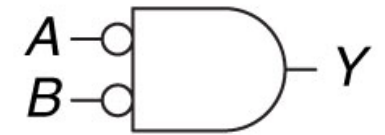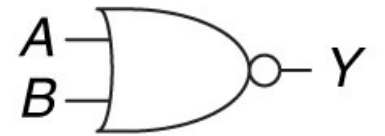

$$Y = \overline{A+B} = \bar{A} \bar{B}$$


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

De Morgan's Theorem

This is why you *need to be careful with your NOTs*

Note that $(AB)'$ is *not* the same as $A'B'$



NAND

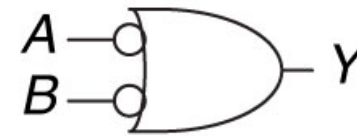

$$Y = \overline{AB} = \overline{A} + \overline{B}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR

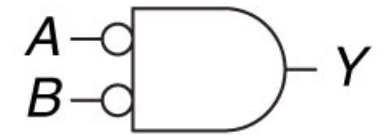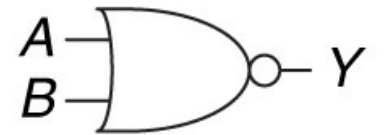

$$Y = \overline{A+B} = \overline{A} \overline{B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Putting it into practice

Simplify $Y = (A' B') + (A'B)$

	Theorem		Dual	Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + (B \bullet D) = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2} \dots)$	De Morgan's Theorem

Simplification

From Sum-of-Products form, typically look for $PA + P'A = A$

Implicant: Product of one or more literals

Minimized: uses the fewest possible implicants

(If several with same number of implicants, minimal one has the fewest literals.)

Simplification

Key: Sometimes we might expand an implicant to minimize an equation.

$$\text{Simplify: } Y = A'B'C' + AB'C' + AB'C$$

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	
1	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B} C$	T8: Distributivity
2	$\overline{B} \overline{C}(1) + A \overline{B} C$	T5: Complements
3	$\overline{B} \overline{C} + A \overline{B} C$	T1: Identity



Simplification

You have an A to remove from the first two terms, and you have a C to remove from the last two terms.

Do you have to choose one or the other?

$$\text{Simplify: } Y = A'B'C' + AB'C' + AB'C$$

Step	Equation	Justification
	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	
1	$\overline{A} \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} \overline{C} + A \overline{B} C$	T3: Idempotency
2	$\overline{B} \overline{C}(\overline{A} + A) + A \overline{B}(\overline{C} + C)$	T8: Distributivity
3	$\overline{B} \overline{C}(1) + A \overline{B}(1)$	T5: Complements
4	$\overline{B} \overline{C} + A \overline{B}$	T1: Identity

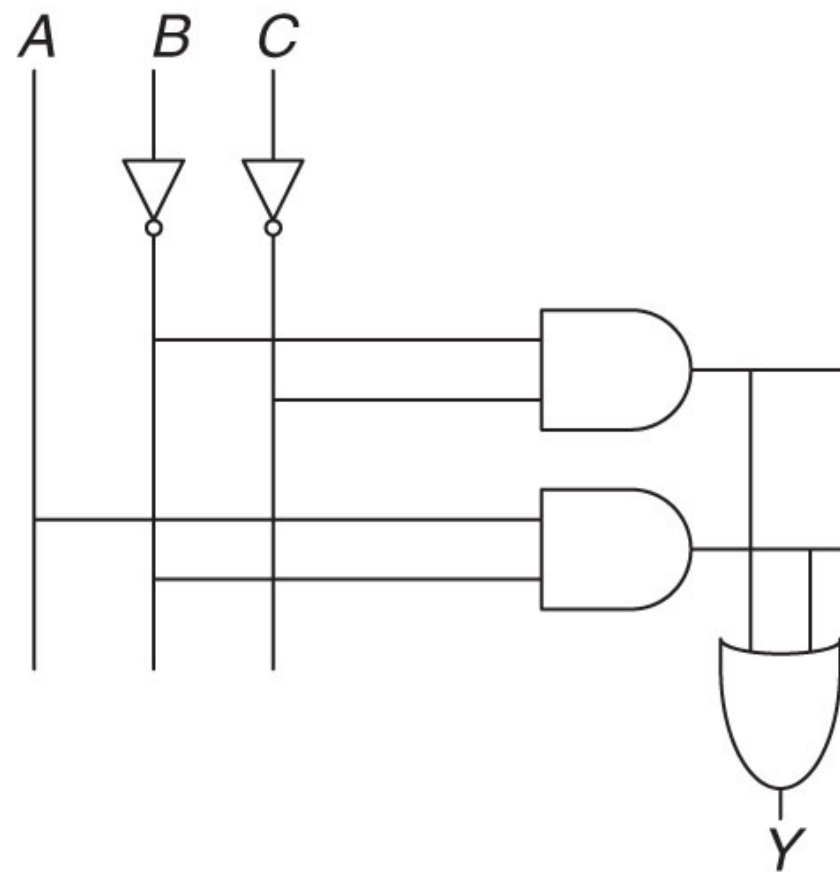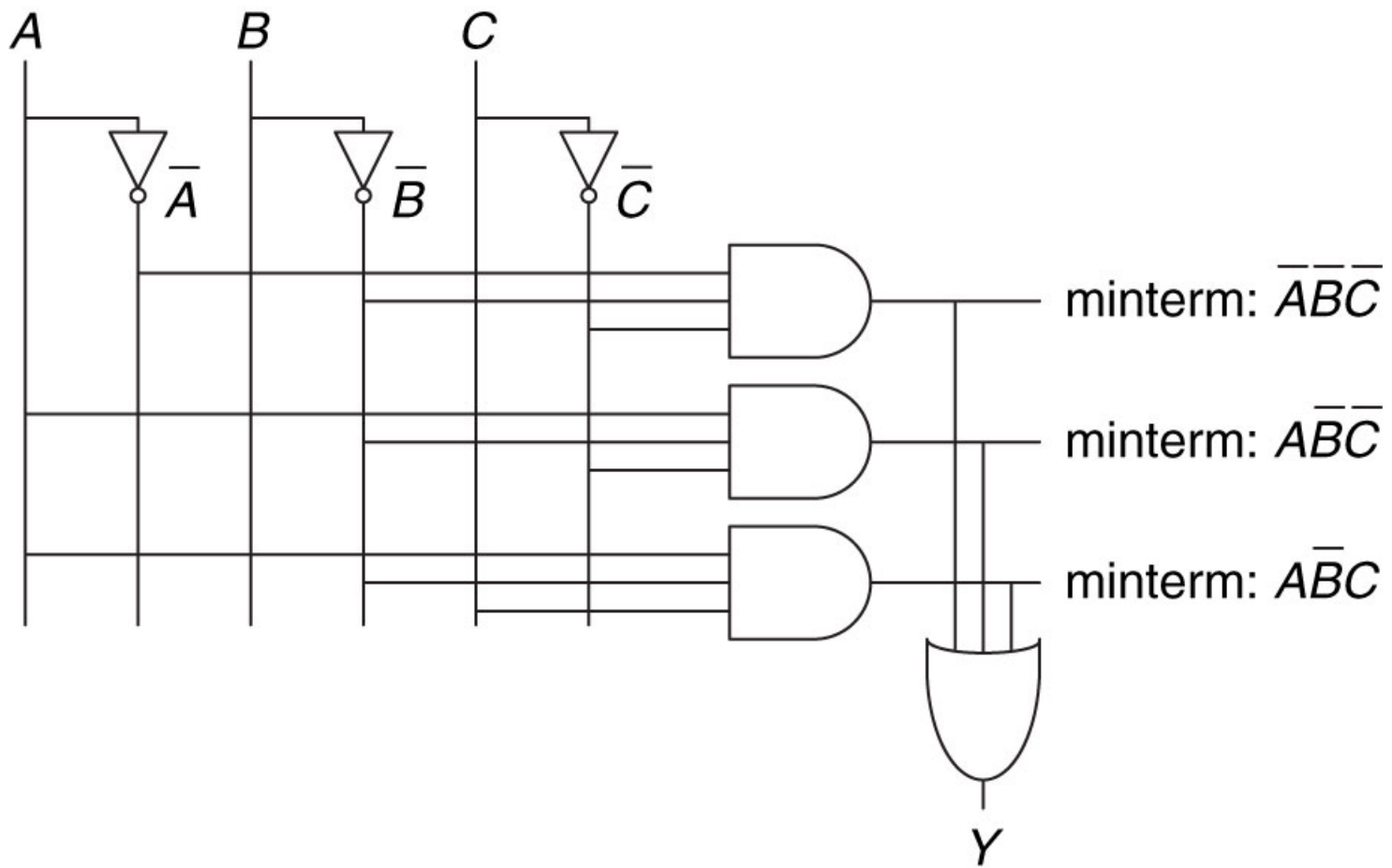

Why Simplify?

1. Reduce the number of gates.
2. Smaller/Cheaper Circuits
3. Maybe faster.

Yes, but this process seems *ad-hoc*.

We will examine another technique, Karnaugh Maps, in a future lecture to make the process more direct.

Hardware Reduction

Sum-of-Products is two-level logic.


Might have circuits with three levels instead.

- Possibly simplifies a circuit.


- More complex logic available.

3-Input XOR

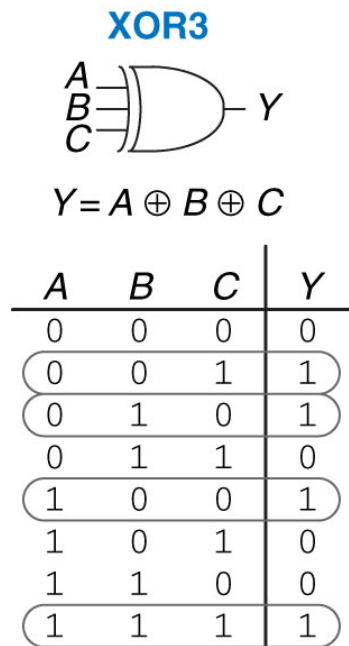
$$Y = \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} \overline{C} + ABC$$



(a)

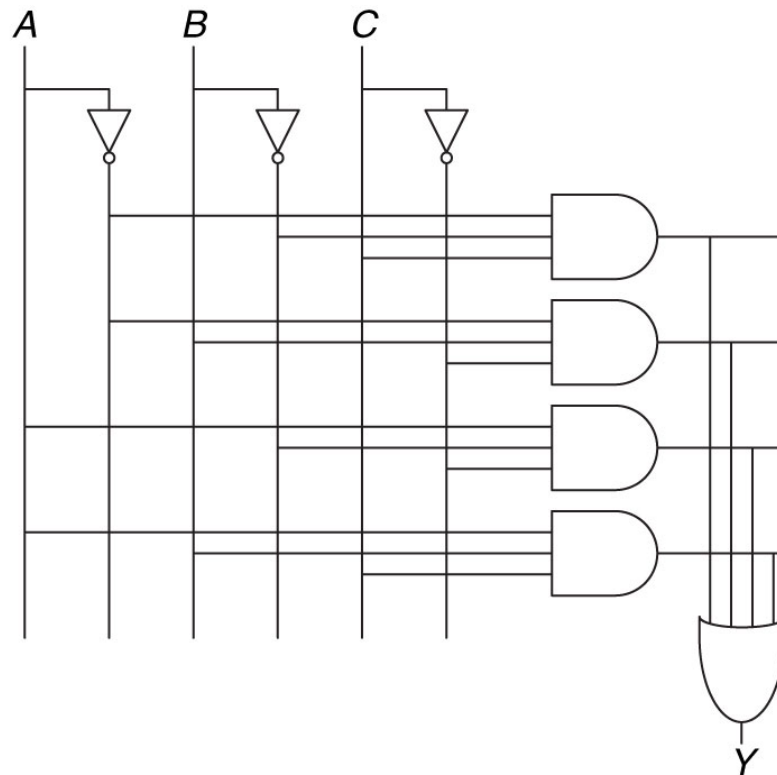

(b)

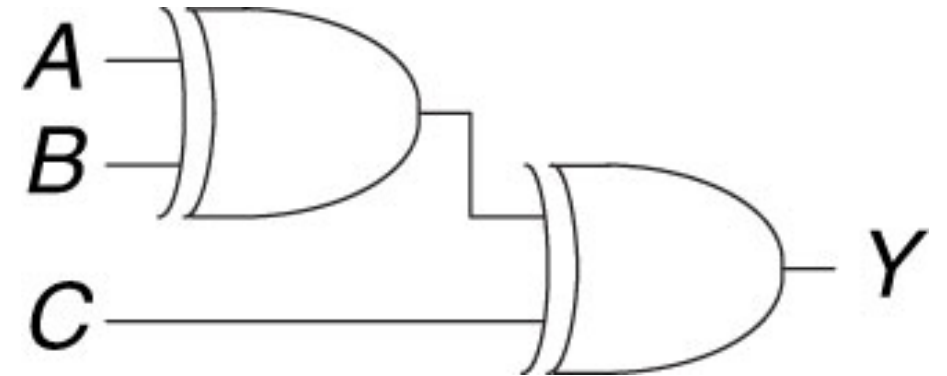

8-Input XOR

8 input XOR needs 128 eight-input AND gates and 1 128-input OR gate.

Can do the same with 7 two-input XOR gates.

