

# Logically Complete

Set of logical operators that can express all possible truth table values by combining into a Boolean expression

For example: {AND, NOT}

May not be the simplest equations, but still a useful property to know and understand.

Equivalently, set of *gates* that can be used to build any circuit

# Logically Complete

Why do we care?

This is a guarantee that, as long as we start out with some minimal set of gates, there is no (combinational) circuit that we won't be able to build

# Logically Complete

- How do we know that {AND, OR, NOT} is logically complete?
  - We can express any truth table in SOP form!

# Logically Complete

- What if we want to show another set is logically complete?
  - For example, given that {AND, OR, NOT} is logically complete, how can we show that {AND, NOT} is logically complete?

# Logically Complete

- What if we want to show another set is logically complete?
  - For example, given that {AND, OR, NOT} is logically complete, how can we show that {AND, NOT} is logically complete?
- Build an OR gate using only {AND, NOT}

# Logically Complete

- In general, if set  $S$  is logically complete, we can show that set  $T$  is logically complete by using  $T$  to build every element of  $S$ .