

Converting Between Forms

Converting Between Forms

- Truth tables, Boolean algebra, and combinational circuits all represent the same thing
- What does it mean for a particular truth table to be equivalent to a particular Boolean expression?

A	B	Y
0	0	0
0	1	1
1	0	0
1	1	1

Matches:

$$A' B + AB$$

$$B (A + A')$$

$$B$$

Not matches:



$$A' B$$

$$AB$$

$$B + (AB')$$


A	B	Y
0	0	0
0	1	1
1	0	0
1	1	1


Matches:

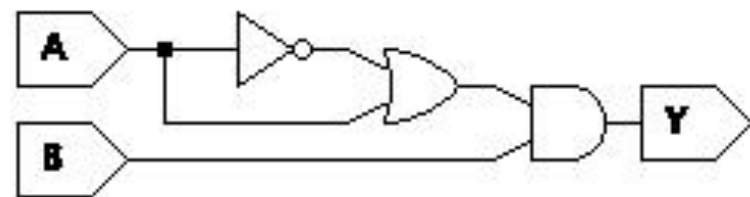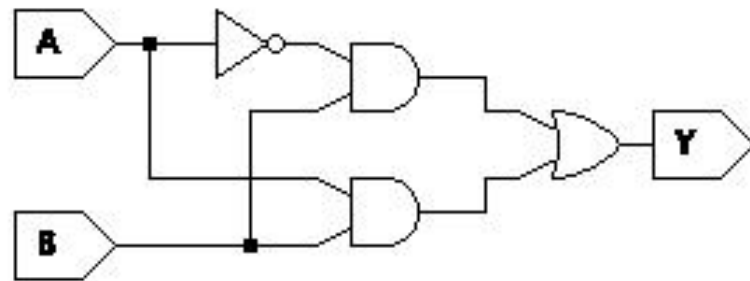

Converting Between Forms

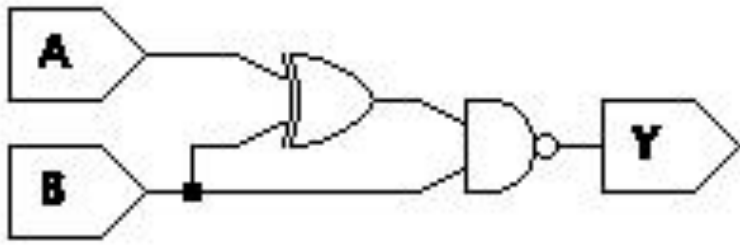- Converting to a truth table is “easy” – just plug in all inputs
 - Downside: there can be a lot of inputs
- What about converting between Boolean expressions and circuits?





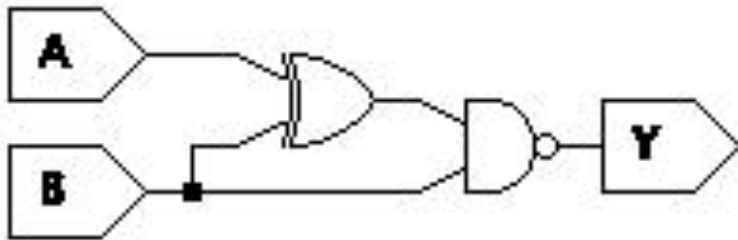

$$((A \text{ xor } B) Y)'$$

$$(A + B)' + AB$$

$$(A + B)' + AB$$

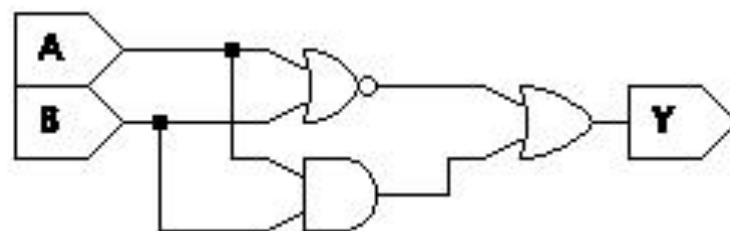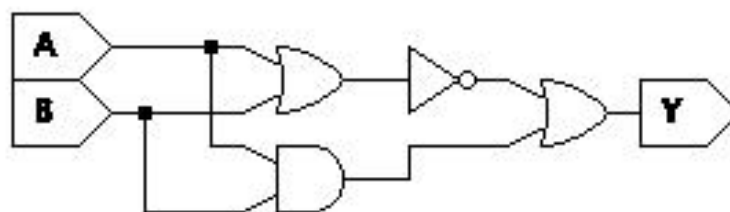

Converting Between Forms

- What about converting between Boolean expressions and circuits?
 - Also straightforward, just "reading them off"
 - Need to be careful about order of operations and groupings
 - Unlike converting to truth tables, there is no one correct answer